

Digital Logic Design

CPCS-211

By

Aman Ullah

Lecture No 34

Design Of Synchronous Counters

Today's Topics

In this lecture we will cover the following

- Design of Synchronous Counters

Design of Synchronous Counters

- Synchronous counters are sequential circuits that need clock input to count some sequence of numbers.
- Most counters are devices with no data input that go through a fixed
- sequence of states on successive clocks.
- For example, a 4-bit binary counter cycles through the sequence

0 1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 0 1 . . .

- It needs four flip flops because the largest number in this sequence is 15 whose binary is 1111.

Example (4-Bit Binary Counter)


- We want to design a 4-bit binary counter that goes from 0 to 1, 1 to 2, and so on 14 to 15 and then 15 to 0.
- The state table and the truth table for this counter are the same; they have 16 rows (for numbers 0 to 15), 4 input columns (for current number), and 4 output columns (for next number), as shown in the following Table.
- As can be seen, the next state for state 0 (0000) is 1 (0001), for 1 is 2, and so forth, until the next state for 15 (1111) is 0 (0000).
- We shall construct this counter using D-flip flop.
- We know that for D-flip flop, the characteristic equation is
$$D = Q(t+1) = Q^*$$

Example (Contd...)


<u>Input</u>				<u>Output</u>			
A	B	C	D	A*	B*	C*	D*
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	1	0	1	0
1	0	1	0	1	0	1	1
1	0	1	1	1	1	0	0
1	1	0	0	1	1	0	1
1	1	0	1	1	1	1	0
1	1	1	0	1	1	1	1
1	1	1	1	0	0	0	0

 Example (Contd...)

- Now we shall draw K-maps for next state functions A^* , B^* , C^* and D^* as.




$$A^* = AB' + AC' + AD' + A'BCD$$

 


$$B^* = BC' + BD' + B'CD$$

Example (Contd...)

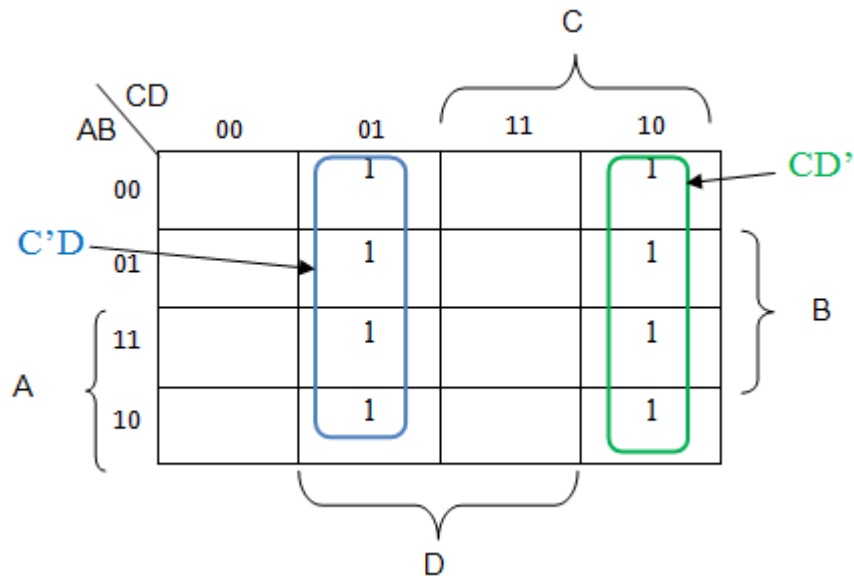

$$C^* = C'D + CD'$$

 

$$D^* = D'$$

Example (Contd...)

- So, the inputs for all four D-flip flops are:

$$D_A = A^* = AB' + AC' + AD' + A'BCD$$

$$D_B = B^* = BC' + BD' + B'CD$$

$$D_C = C^* = C'D + CD'$$

$$D_D = D^* = D'$$

- This solution would require 12 gates (9 AND gates and 3 OR gates) with 30 gate inputs.
- If we have Exclusive-OR gates available, we could simplify the expressions to

$$\begin{aligned} D_A = A^* &= A(B' + C' + D') + A'BCD = A(BCD)' + A'(BCD) \\ &= A \oplus BCD \end{aligned}$$

$$D_B = B^* = B(C' + D') + B'CD = B(CD)' + B'(CD) = B \oplus CD$$

$$D_C = C^* = C'D + CD' = C \oplus D$$

$$D_D = D^* = D'$$

- This would only require 2 AND gates and 3 Exclusive-OR gates.

Example (4-Bit Binary Counter)

- We want to design the same 4-bit binary counter that goes from 0 to 1, 1 to 2, and so on 14 to 15 and then 15 to 0.
- As can be seen, the next state for state 0 (0000) is 1 (0001), for 1 is 2, and so forth, until the next state for 15 (1111) is 0 (0000).
- We shall construct this counter using JK-flip flops.
- We know that for JK-flip flop, the excitation table is

Q	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

- Using this excitation table, we construct the following input table (or state table) for the required counter as:

Example (Contd...)

Current States				Next States				Flip Flop Inputs							
A	B	C	D	A*	B*	C*	D*	J _A	K _A	J _B	K _B	J _C	K _C	J _D	K _D
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	1	0	1	0	X	0	0	X	1	X	X	1
1	0	1	0	1	0	1	1	X	0	0	X	X	0	1	X
1	0	1	1	1	1	0	0	X	0	1	X	X	1	X	1
1	1	0	0	1	1	0	1	X	0	X	0	0	X	1	X
1	1	0	1	1	1	1	0	X	0	X	0	1	X	X	1
1	1	1	0	1	1	1	1	X	0	X	0	X	0	1	X
1	1	1	1	0	0	0	0	X	1	X	1	X	1	X	1

Table 7.6


q	q^*
0	0
0	1
1	0
1	1

Example (Contd...)

- Next step is to draw K-maps for J_A , K_A , J_B , K_B , J_C , K_C , J_D and K_D
- In order to save time, we can compare all the columns with one another and conclude that
$$J_A = K_A = BCD$$
$$J_B = K_B = CD$$
$$J_C = K_C = D$$
$$J_D = K_D = 1$$
- Thus the circuit for the given 4-bit counter, using four JK-flip flops is as follows:

Example (Contd...)

Figure 7.6 A 4-bit counter.*

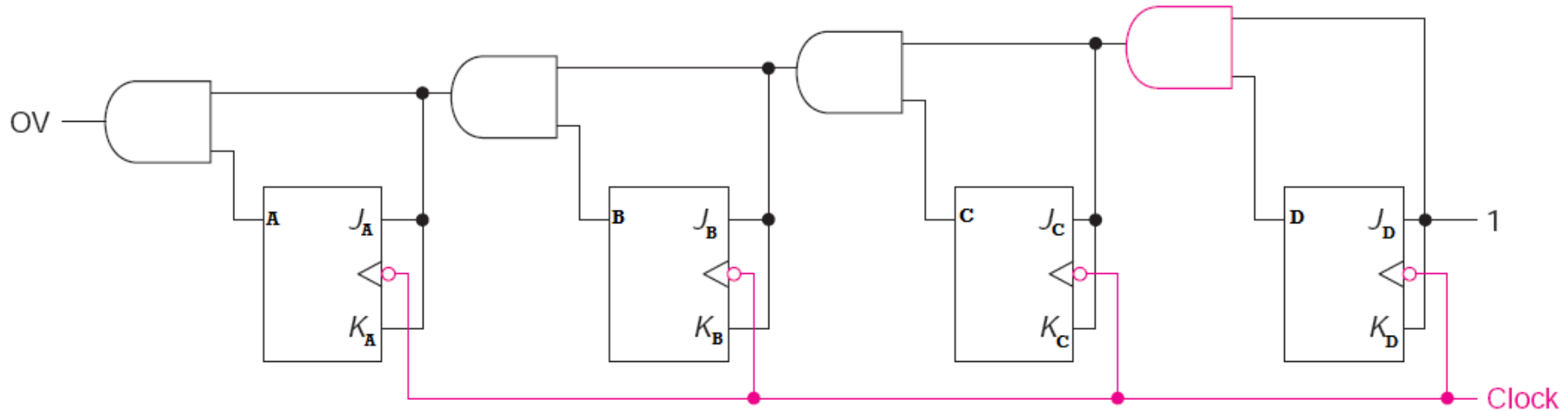

- The first AND gate is not necessary if this is a stand-alone counter; the output of the “D” flip flop would be connected directly to J_C and K_C .
- The OV output is 1 when the counter is in state 15 (1111). OV could be connected to the JK inputs of another flip flop or, if we built two 4 flip flop circuits like the one above, we could connect the OV output of one to the input where a 1 is now connected to construct an 8-bit counter.

Example (An Up/Down Counter)

- An up/down counter is a one that can count in either direction, depending upon a control input.
- We will label that control input x , such that the counter counts up when $x = 0$ and counts down when $x = 1$.
- We shall design this counter by using JK-flip flops.
- The state table for such a counter is shown below:

Example (Contd...)


Current State				Next State			Flip Flop Inputs					
X	A	B	C	A*	B*	C*	J _A	K _A	J _B	K _B	J _C	K _C
0	0	0	0	0	0	1	0	X	0	X	1	X
0	0	0	1	0	1	0	0	X	1	X	X	1
0	0	1	0	0	1	1	0	X	X	0	1	X
0	0	1	1	1	0	0	1	X	X	1	X	1
0	1	0	0	1	0	1	X	0	0	X	1	X
0	1	0	1	1	1	0	X	0	1	X	X	1
0	1	1	0	1	1	1	X	0	X	0	1	X
0	1	1	1	0	0	0	X	1	X	1	X	1
1	0	0	0	1	1	1	1	X	1	X	1	X
1	0	0	1	0	0	0	0	X	0	X	X	1
1	0	1	0	0	0	1	0	X	X	1	1	X
1	0	1	1	0	1	0	0	X	X	0	X	1
1	1	0	0	0	1	1	X	1	1	X	1	X
1	1	0	1	1	0	0	X	0	0	X	X	1
1	1	1	0	1	0	1	X	0	X	1	1	X
1	1	1	1	1	1	0	X	0	X	0	X	1

Table


q
0
0
1
1

 Example (Contd...)

- The K-maps for J_A , K_A , J_B , K_B , J_C and K_C are as follows:





$$J_A = X'BC + XB'C'$$

 

$$K_A = X'BC + XB'C'$$


Example (Contd...)

  


- $J_B = XC' + X'C$

$$K_B = XC' + X'C$$

Example (Contd...)

 

$$J_C = 1$$

 


$$K_C = 1$$

Example (Contd...)

- A block diagram for up/down counter is shown in Figure 7.7.

Figure 7.7 An up/down counter.

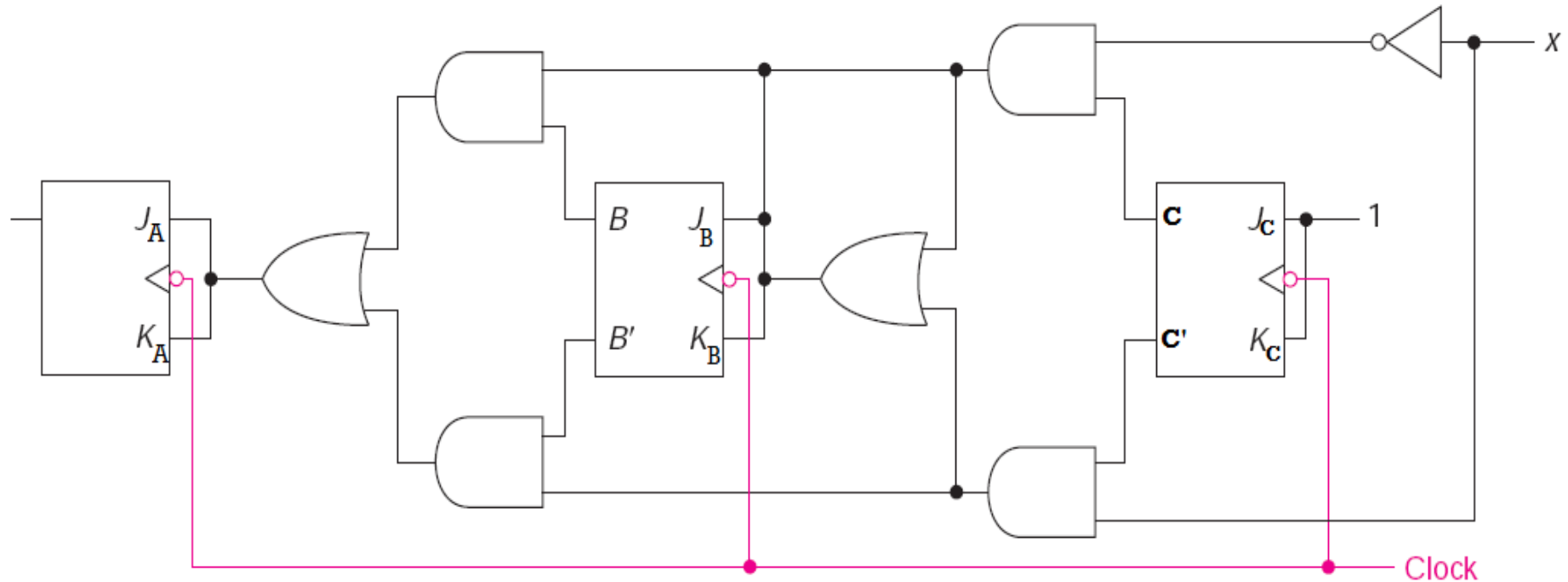

Example (Decimal Counter)

- We will look next at a decimal or decade counter, one that goes through the sequence
0 1 2 3 4 5 6 7 8 9 0 1 . . .
- We shall design this counter using JK-flip flops.
- The state (truth) table is similar to that for the binary counter, as seen below:

Example (Contd...)

Current States				Next States				Flip Flop Inputs							
A	B	C	D	A*	B*	C*	D*	J _A	K _A	J _B	K _B	J _C	K _C	J _D	K _D
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	0	0	0	0	X	0	0	X	0	X	X	1
1	0	1	0	Don't Care				X	X	X	X	X	X	X	X
1	0	1	1	Don't Care				X	X	X	X	X	X	X	X
1	1	0	0	Don't Care				X	X	X	X	X	X	X	X
1	1	0	1	Don't Care				X	X	X	X	X	X	X	X
1	1	1	0	Don't Care				X	X	X	X	X	X	X	X
1	1	1	1	Don't Care				X	X	X	X	X	X	X	X

Table 7.6

q	q^*
0	0
0	1
1	0
1	1

Example (Contd...)

- Next step is to draw K-maps for J_A , K_A , J_B , K_B , J_C , K_C , J_D and K_D
- It is left as an exercise for the students.
- We shall get the following input equations for all four flip flops.
 $J_A = BCD$, $K_A = D$
 $J_B = K_B = CD$
 $J_C = A'D$, $K_C = D$
 $J_D = K_D = 1$
- Thus the circuit for the required decimal counter, using four JK-flip flops is as follows:

Example (Contd...)

- Circuit for the required decimal counter is left as an exercise for the students.

Example


- We will next design a counter that goes through some sequence of states that are not in numeric order
0 3 2 4 1 5 7 and repeat
- We shall design this counter by using D, SR, T and JK-flip flops.
- Note that the cycle is 7 states; it never goes through state 6 (which will be treated as don't care).
- We can now draw the state table (in any order) or go directly to the truth table, including a row for the unused state.
- The combined state table for SR and T-flip flop inputs for such a counter is shown below:

Example (Contd...)


q_1	q_2	q_3	q_1^\star	q_2^\star	q_3^\star	S_1	R_1	S_2	R_2	S_3	R_3	T_1	T_2	T_3
0	0	0	0	1	1	0	X	1	0	1	0	0	1	1
0	0	1	1	0	1	1	0	0	X	X	0	1	0	0
0	1	0	1	0	0	1	0	0	1	0	X	1	1	0
0	1	1	0	1	0	0	X	X	0	0	1	0	0	1
1	0	0	0	0	1	0	1	0	X	1	0	1	0	1
1	0	1	1	1	1	X	0	1	0	X	0	0	1	0
1	1	0	X	X	X	X	X	X	X	X	X	X	X	X
1	1	1	0	0	0	0	1	0	1	0	1	1	1	1

We shall now first construct K-maps for S_1 , R_1 , S_2 , R_2 , S_3 and R_3


Example (Contd...)

 


$$S_1 = q'_2 q_3 + q_2 q'_3$$

 

$$R_1 = q'_2 q'_3 + q_2 q_3$$

 

$$S_2 = q'_1 q'_2 q'_3 + q_1 q'_2 q_3$$

 

$$R_2 = q_1 q_2 + q_2 q'_3$$

Example (Contd...)

q ₂ q ₃		q ₂			
		00	01	11	10
q ₁	0	1	X		
	1	1	X		X

Diagram illustrating a Karnaugh map for a 3-variable function. The map is a 2x4 grid. The columns are labeled 00, 01, 11, and 10. The rows are labeled 0 and 1. The cells contain values: (0,0)=1, (0,1)=X, (1,0)=1, (1,1)=X, (1,2)=, (1,3)=X. A green box highlights the cells (0,0), (0,1), (1,0), and (1,1). An arrow points from the label q₂ to the bottom-left corner of the green box. Another arrow points from the label q₃ to the bottom-right corner of the green box.

$$S_3 = q'_2$$

q ₂ q ₃		q ₂			
		00	01	11	10
q ₁	0			1	X
	1			1	X

Diagram illustrating a Karnaugh map for a 3-variable function. The map is a 2x4 grid. The columns are labeled 00, 01, 11, and 10. The rows are labeled 0 and 1. The cells contain values: (0,3)=1, (0,4)=X, (1,3)=1, (1,4)=X. A green box highlights the cells (0,3), (0,4), (1,3), and (1,4). An arrow points from the label q₂ to the bottom-right corner of the green box. Another arrow points from the label q₃ to the bottom-left corner of the green box.

$$R_3 = q_2$$


- The circuit for the required counter using SR-flip flops is as follows:

Example (Contd...)


- Left as an exercise for the students:

 Example (Contd...)


- Now K-maps for T_1 , T_2 and T_3 are as follows:


 
$$T_1 = q'_1 q'_2 q_3 + q_1 q_2 + q_1 q'_3 + q_2 q'_3$$



$$T_2 = q_1 q_3 + q'_1 q'_3$$

 

$$T_3 = q_2 q_3 + q'_2 q'_3$$

Example (Contd...)

- The circuit of required counter using T-flip flops is as follows:
- Left as an exercise for the students

Example (Contd...)

- Now finally we shall construct the circuit for the required counter using JK-flip flops.
- For this, the following table gives the JK-flip flop inputs.

Current State			Next State			Flip Flop Inputs					
q_1	q_2	q_3	q_1^*	q_2^*	q_3^*	J_1	K_1	J_2	K_2	J_3	K_3
0	0	0	0	1	1	0	X	1	X	1	X
0	0	1	1	0	1	1	X	0	X	X	0
0	1	0	1	0	0	1	X	X	1	0	X
0	1	1	0	1	0	0	X	X	0	X	1
1	0	0	0	0	1	X	1	0	X	1	X
1	0	1	1	1	1	X	0	1	X	X	0
1	1	0	X	X	X	X	X	X	X	X	X
1	1	1	0	0	0	X	1	X	1	X	1

- The K-maps for J_1 , K_1 , J_2 , K_2 , J_3 and K_3 are as follows:

Tabl

q


0

0


1

1


Example (Contd...)

 


$$J_1 = q'_2 q_3 + q_2 q'_3$$

 

$$K_1 = q_2 + q'_3$$

 

$$J_2 = q_1 q_3 + q'_1 q'_3$$

 

$$K_2 = q_1 + q'_3$$

Example (Contd...)

q ₂ q ₃		q ₂			
		00	01	11	10
q ₁	0	1	X	X	
	1	1	X	X	X

Diagram illustrating the Karnaugh map for the J₃ input. The map shows the values of J₃ for different combinations of q₁ and q₂q₃. The values are 1 for (q₁=0, q₂q₃=00) and (q₁=1, q₂q₃=00), and X for (q₁=0, q₂q₃=01), (q₁=1, q₂q₃=01), (q₁=0, q₂q₃=11), (q₁=1, q₂q₃=11), and (q₁=1, q₂q₃=10). A green box highlights the cells where J₃ = 1, and an arrow points to the cell (q₁=1, q₂q₃=00) with the label q'₂.

$$J_3 = q'_2$$

q ₂ q ₃		q ₂			
		00	01	11	10
q ₁	0	X		1	X
	1	X		1	X

Diagram illustrating the Karnaugh map for the K₃ input. The map shows the values of K₃ for different combinations of q₁ and q₂q₃. The values are X for (q₁=0, q₂q₃=00), (q₁=1, q₂q₃=00), (q₁=0, q₂q₃=10), and (q₁=1, q₂q₃=10), and 1 for (q₁=0, q₂q₃=11) and (q₁=1, q₂q₃=11). A green box highlights the cells where K₃ = 1, and an arrow points to the cell (q₁=1, q₂q₃=10) with the label q₂.

$$K_3 = q_2$$

- The circuit for the required counter using JK-flip flops is as follows:

Example (Contd...)

- Left as an exercise for the students

Dealing with Don't Care States

- We can determine what would happen by assuming we are in state 110.
- Thus, we would put $q_1 = 1$, $q_2 = 1$, and $q_3 = 0$ in the equations of flip flop inputs.
- For example, For D-flip flops, we would get

$$D_1 = q'_2 q_3 + q_2 q'_3 = 00 + 11 = 1$$

$$D_2 = q'_1 q'_2 q'_3 + q'_1 q_2 q_3 + q_1 q'_2 q_3 = 001 + 011 + 100 = 0$$

$$D_3 = q'_2 = 0$$


- It means that, the system would go to state 4 (100) on the first clock and continue through the sequence from there.

Note:

- With SR-flip flops, it also goes to state 4, to state 2 with T-flip flops and to state 0 with JK-flip flops.

Dealing with Don't Care States (Contd...)

 - A state diagram, showing the behavior of the system designed with D or SR flip flops, including what happens if the system starts in the unused state, is shown next.



Thanks

